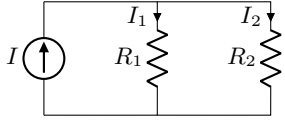
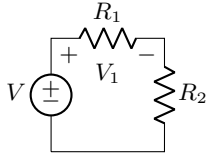


**Review***Current division*

$$I_1 = \frac{R_2}{R_1 + R_2} I$$

*Voltage division*

$$V_1 = \frac{R_1}{R_1 + R_2} V$$

**Capacitors and Inductors**

$$q(t) = C v(t) \quad i_c(t) = C \frac{dv(t)}{dt} \quad v_c(t) = v_c(t_0) + \frac{1}{C} \int_{t_0}^t i_c(x) dx$$

$$p_c(t) = v_c(t) i_c(t) \quad E_c(t) = \frac{1}{2} C V^2 = \frac{Q^2}{2C} = \frac{1}{2} Q V$$

$$L = \frac{\lambda(t)}{i_L(t)} \quad v_L(t) = L \frac{di(t)}{dt} \quad i_L(t) = i_L(t_0) + \frac{1}{L} \int_{t_0}^t i_L(x) dx$$

$$p_L(t) = v_L(t) i_L(t) \quad E_L(t) = \frac{1}{2} L [i_L(t)]^2$$


$$C_s = \left( \sum_{i=1}^N \frac{1}{C_i} \right)^{-1} \quad C_p = \sum_{i=1}^N C_i \quad L_s = \sum_{i=1}^N L_i \quad L_p = \left( \sum_{i=1}^N \frac{1}{L_i} \right)^{-1}$$

**General Solution of First-Order Circuits**

$$\dot{x}(t) + ax(t) = A, \text{ where } x(t) = K_1 + K_2 e^{-t/\tau}$$

$$K_1 = \frac{A}{a} \quad \tau = \frac{1}{a} \quad K_2 = x(0) - K_1$$

$$v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau} \quad i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

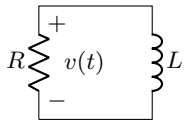Compute  $R_{Th}$  from view of energy storage device to find  $\tau$ .**Transient Behaviour of First-Order Circuits***Discharging RL Circuit*

$$L \frac{di(t)}{dt} + Ri(t) = 0$$


$$v_c(0^-) = v_c(0^+)$$

$$i(t) = i(0^+) e^{-t/\tau}$$

$$\tau = L/R$$

$$E_L(0^+) = \frac{1}{2} L \left( \frac{V_s}{R} \right)^2$$

$$E_L(\infty) = 0$$

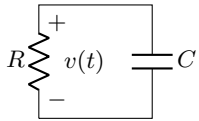*Discharging RC Circuit*

$$C \frac{dv(t)}{dt} + \frac{v(t)}{R} = 0$$


$$i_L(0^-) = i_L(0^+)$$

$$v(t) = v(0^+) e^{-t/\tau}$$

$$\tau = RC$$

$$E_C(0^+) = \frac{1}{2} C v(0^+)$$

$$E_C(\infty) = 0$$

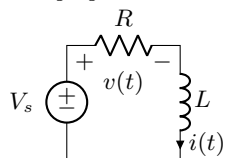
**Step Response of First-Order Circuits***Charging RL Circuit*

$$L \frac{di(t)}{dt} + Ri(t) = V_s$$

$$i(t) = \frac{V_s}{R} (1 - e^{-t/\tau})$$

$$\tau = L/R$$

$$v_L(t) = V_s e^{-t/\tau}$$

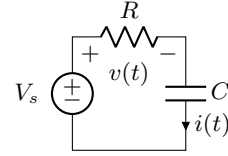*Charging RC Circuit*

$$C \frac{dv(t)}{dt} + \frac{v(t) - V_s}{R} = 0$$

$$i(t) = \frac{V_s}{R} (1 - e^{-t/\tau})$$

$$\tau = RC$$

$$v(t) = V_s (1 - e^{-t/\tau})$$

**General Solution of Second-Order Circuits**

$$\ddot{x}(t) + a_1 \dot{x}(t) + a_2 x(t) = A, \text{ where } x(t) = x_p(t) + x_c(t)$$

$$x_p(t) = \frac{A}{a_2}$$

$$x_c(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

$$x(0) = \frac{A}{a_2} + K_1 + K_2$$

$$\dot{x}(0) = K_1 s_1 + K_2 s_2$$

Obtain  $\dot{x}(0)$  from ODE of circuit


$$\text{Characteristic eq: } s^2 + 2\zeta\omega_0 s + \omega_0^2 = 0$$

$$\zeta > 1: x_c(t) = K_1 e^{-\omega_0(\zeta - \sqrt{\zeta^2 - 1})t} + K_2 e^{-\omega_0(\zeta + \sqrt{\zeta^2 - 1})t}$$

$$\zeta = 1: x_c(t) = (B_1 + B_2 t) e^{-\zeta\omega_0 t}$$

$$\zeta < 1: x_c(t) = e^{-\sigma t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t)$$


$$\sigma = \omega_0 \zeta, \quad \omega_d = \omega_0 \sqrt{1 - \zeta^2}$$

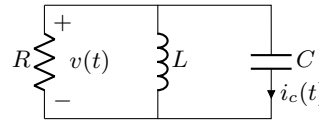**Second-Order Circuit w/o Source***Parallel RLC Circuit*

$$v(0) = K_1 + K_2$$

$$\frac{dv(0)}{dt} = \frac{1}{C} i_c(t) = K_1 s_1 + K_2 s_2$$


$$\frac{d^2 v_c(t)}{dt^2} + \frac{1}{RC} \frac{dv_c(t)}{dt} + \frac{1}{LC} v_c(t) = 0$$

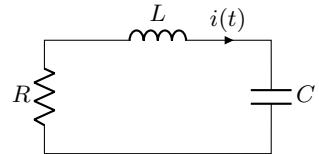*Series RLC Circuit*


$$i(0) = K_1 + K_2$$

$$\frac{di(0)}{dt} = \frac{v_L(0)}{L} = K_1 s_1 + K_2 s_2$$

$$\frac{d^2 i_L(t)}{dt^2} + \frac{R}{L} \frac{di_L(t)}{dt} + \frac{1}{LC} i_L(t) = 0$$

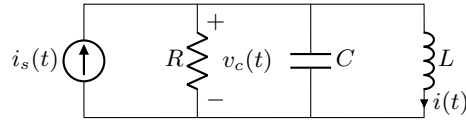**Second-Order w/ Source***Parallel RLC Circuit with Current Source*

$$\frac{d^2 v_c(t)}{dt^2} + \frac{1}{RC} \frac{dv_c(t)}{dt} + \frac{1}{LC} v_c(t) = \frac{1}{C} \frac{di_s(t)}{dt}$$

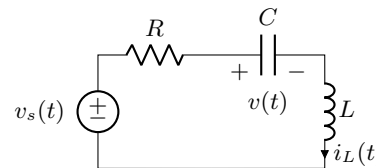*Series RLC Circuit with Voltage Source*

$$\frac{d^2 i_L(t)}{dt^2} + \frac{R}{L} \frac{di_L(t)}{dt} + \frac{1}{LC} i_L(t) = \frac{1}{L} \frac{dv_s(t)}{dt}$$

## Tricky Questions


Set up the 2nd-order eq for  $v_c(t)$ .

$$8 = i_L(t) + i_R(t)$$

$$\Rightarrow i_R(t) = 8 - i_L(t)$$


$$L \frac{di_L(t)}{dt} + v_c(t) - R(8 - i_L(t)) = 0$$
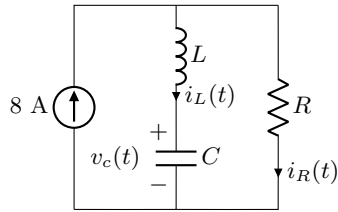
$$\text{But } i_L(t) = i_c(t) = C \frac{dv_c(t)}{dt}$$




$$\text{Therefore, } LC \frac{d^2 v_c(t)}{dt^2} + v_c(t) + RC \frac{dv_c(t)}{dt} = 8R$$

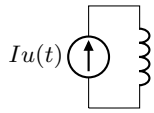
Which circuits do not violate any v-i terminal relationships?




Not allowed

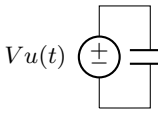

Not allowed

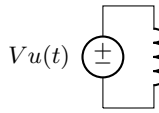

Allowed

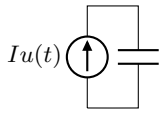

Allowed

## Generalized Phasor

$$x(t) = \text{Re}\{X e^{j\theta} e^{st}\}, \quad s = \sigma + j\omega$$

- $s = 0 \Rightarrow$  dc.  $\sin \mapsto \cos : \sin \theta = \cos(\theta - 90^\circ)$
- $s = \sigma \Rightarrow$  pure exponential.  $\cos \mapsto \sin : \cos \theta = \sin(\theta + 90^\circ)$
- $s = j\omega \Rightarrow$  pure sinusoidal.
- $s = \sigma + j\omega \Rightarrow$  damped sinusoidal.
- $\sigma$  in Np/s,  $\omega$  in rad/s,  $f$  in cycles/s.

$$x(t) = 4e^{-3t} \sin(6t + 10^\circ) \Rightarrow s = -3 + 6j, \quad \bar{x} = 4 \angle -80^\circ$$

	R	L	C
$\bar{Z}(s)$	$R$	$sL$	$1/sC$
$\bar{Y}(s)$	$1/R$	$1/sL$	$sC$

## Transfer Functions

$$H(s) = \frac{Y(s)}{X(s)} = \frac{\text{o/p}}{\text{i/p}} = \frac{\text{forced response}}{\text{forcing fn}}$$

$$\bar{Y}_p = H(s) \bar{X}(s)|_s \Rightarrow y_p(t) = \text{Re}\{\bar{Y}_p e^{st}\}$$


$s$  is complex freq of excitation source.

$$\text{Find } H_1(s) = \frac{\bar{V}_c(s)}{\bar{V}(s)}$$


$$H_1(s) = \frac{\frac{1}{sC}}{R + sL + \frac{1}{sC}}$$

$$\text{Find } H_2(s) = \frac{\bar{I}(s)}{\bar{V}(s)}$$
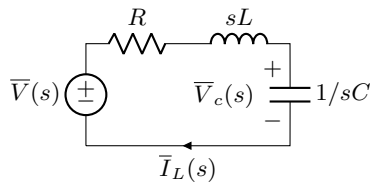
$$H_2(s) = \frac{s/L}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$



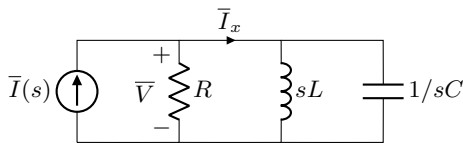Pole plot: need poles (X) and zeros (O) of  $H(s)$ , i.e., critical freqs.



$$\frac{\bar{V}}{\bar{I}} = \frac{1}{\frac{1}{R} + \frac{1}{sL} + sC} = \frac{sL}{s^2 LC + \frac{sL}{R} + 1} = \frac{sL}{\left(\frac{s}{\omega_0}\right)^2 + \left(\frac{s}{\omega_0}\right) \frac{1}{Q} + 1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{\omega_0}{\beta} = \frac{1}{R} \sqrt{\frac{L}{C}}$$


## Frequency Response Analysis

For  $x_i(t) = X_i \cos(\omega t + \theta_i)$  and transfer fn  $H(j\omega) = |H(j\omega)| \angle \theta_H(j\omega)$ , the output is  $\bar{X}_0 = X_i |H(j\omega)| \angle (\theta_i + \theta_H(j\omega))$ .

Freq response plot consists of magnitude plot,  $|H(j\omega)|$  vs  $\omega$ , and phase plot,  $\angle \theta_H(j\omega)$  vs  $\omega$ .

### Low Pass Filter (LPF)

RL Implementation

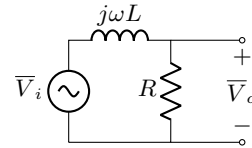


$$H(j\omega) = \frac{\bar{V}_0}{\bar{V}_i} = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega \tau_c}$$

$$\tau_c = L/R$$

$$|\bar{V}_0| \approx |\bar{V}_i| \iff \omega \tau_c \ll 1$$

$$|\bar{V}_0| \ll |\bar{V}_i| \iff \omega \tau_c \gg 1$$

RC Implementation

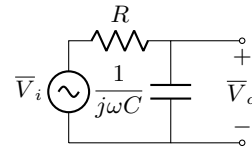

$$H(j\omega) = \frac{\bar{V}_0}{\bar{V}_i} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega \tau_c}$$


$$\tau_c = RC$$

$$|H(j\omega)| = \frac{1}{\sqrt{(\omega \tau_c)^2 + 1}}$$

$$\angle H(j\omega) = \arctan(-\omega \tau_c)$$

### High Pass Filter (HPF)

RC Implementation

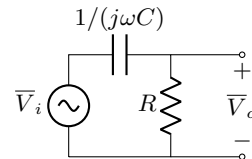


$$H(j\omega) = \frac{\bar{V}_0}{\bar{V}_i} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{1}{1 + \frac{1}{j\omega \tau_c}}$$

$$\tau_c = RC$$

$$|\bar{V}_0| \approx |\bar{V}_i| \iff \omega \tau_c \gg 1$$

$$|\bar{V}_0| \ll |\bar{V}_i| \iff \omega \tau_c \ll 1$$

RL Implementation

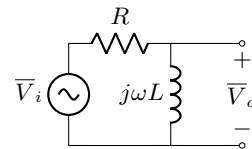


$$H(j\omega) = \frac{\bar{V}_0}{\bar{V}_i} = \frac{j\omega L}{R + j\omega L} = \frac{1}{1 + \frac{1}{j\omega \tau_c}}$$

$$\tau_c = L/R$$

$$|H(j\omega)| = \frac{1}{\sqrt{\left(\frac{1}{\omega \tau_c}\right)^2 + 1}}$$

$$\angle H(j\omega) = \arctan\left(\frac{1}{\omega \tau_c}\right)$$

### Band Pass Filter (BPF)

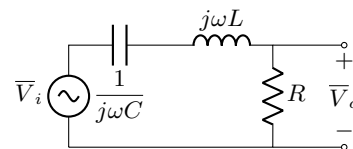

$$\tau_{c1} = RC$$

$$\tau_{c2} = L/R$$

$$H(j\omega) = \frac{\bar{V}_0}{\bar{V}_i} = \frac{R}{(j\omega C)^{-1} + j\omega L + R} = \frac{1}{(j\omega \tau_{c1})^{-1} + j\omega \tau_{c2} + 1}$$

$$= \frac{j\omega \tau_{c1}}{1 + 2\zeta(j\omega \tau_0) + (j\omega \tau_0)^2} \quad \tau_0 = \sqrt{\tau_{c1} \tau_{c2}} = \sqrt{LC}$$

$$\zeta = \frac{\tau_{c1}}{2\tau_0} = \frac{R}{2} \sqrt{\frac{C}{L}} = \frac{1}{2Q}$$

$$\omega = \frac{1}{\sqrt{LC}} \Rightarrow |\bar{V}_0| \approx |\bar{V}_i|$$

$$\omega \ll 1/\tau_{c1} \Rightarrow |\bar{V}_0| \ll |\bar{V}_i|$$

$$\omega \gg 1/\tau_{c2} \Rightarrow |\bar{V}_0| \ll |\bar{V}_i|$$

$$|H(j\omega)| = \frac{1}{\sqrt{\left(\omega \tau_{c2} - \frac{1}{\omega \tau_{c1}}\right)^2 + 1}}$$

$$\angle H(j\omega) = \arctan\left(\frac{1}{\omega \tau_{c1}} - \omega \tau_{c2}\right)$$

## Cutoff Frequency

$$|H(j\omega_c)| = \frac{H_{\max}}{\sqrt{2}} \quad H_{\max} = 1$$

$$\text{LPF: } |H(j\omega_c)| = \frac{1}{\sqrt{(\omega\tau_c)^2 + 1}} = \frac{1}{\sqrt{2}} \Rightarrow \omega_c = \frac{1}{\tau_c}$$

$$\text{HPF: } |H(j\omega_c)| = \frac{1}{\sqrt{\left(\frac{1}{\omega\tau_c}\right)^2 + 1}} = \frac{1}{\sqrt{2}} \Rightarrow \omega_c = \frac{1}{\tau_c}$$

$$\text{RL: } f_c = \frac{R}{2\pi L}, \quad \text{RC: } f_c = \frac{1}{2\pi RC}, \quad \text{LPF and HPF have same } f_c$$

## Parameters for Series BPF

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad Z_c = Z_L \text{ at } \omega = \omega_0$$

$$\beta = \omega_{c2} - \omega_{c1} = \frac{R}{L} \quad Q = \frac{\omega_0}{\beta} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\begin{aligned} \omega_{c1} &= -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2} \\ &= \omega_0 \left( -\frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right) = -\frac{1}{2\tau_{c2}} + \sqrt{\left(\frac{1}{2\tau_{c2}}\right)^2 + \frac{1}{\tau_{c1}\tau_{c2}}} \end{aligned}$$

$$\begin{aligned} \omega_{c2} &= \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2} \\ &= \omega_0 \left( \frac{1}{2Q} + \sqrt{\left(\frac{1}{2Q}\right)^2 + 1} \right) = \frac{1}{2\tau_{c2}} + \sqrt{\left(\frac{1}{2\tau_{c2}}\right)^2 + \frac{1}{\tau_{c1}\tau_{c2}}} \end{aligned}$$

## Resonance for BPF

	Series RLC	Parallel RLC
$\omega_0$	$1/\sqrt{LC}$	$1/\sqrt{LC}$
$Q$	$\frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC} = \frac{1}{R} \sqrt{\frac{L}{C}}$	$\frac{R}{\omega_0 L} = \omega_0 RC = R \sqrt{\frac{C}{L}}$
$\beta$	$R/L$	$1/(RC)$
Other	$ \bar{V}_L  = Q \bar{V}_s $ $ \bar{V}_c  = Q \bar{V}_s $ $\bar{V}_L + \bar{V}_c = 0$ $\Rightarrow$ Resonant $V$ rise	$ \bar{I}_L  = Q \bar{I}_s $ $ \bar{I}_c  = Q \bar{I}_s $ $\bar{I}_L + \bar{I}_c = 0$ $\Rightarrow$ Resonant $I$ rise

## Bode Plots

Magnitude:  $20 \log |H(j\omega)|$  vs  $\log \omega$

Phase:  $\angle H(j\omega)$  vs  $\log \omega$

### Examples

$$H(j\omega) = K \Rightarrow H_{db} = 20 \log K, \quad \angle H(j\omega) = 0^\circ$$

$$H(j\omega) = (j\omega)^{\pm n} \Rightarrow H_{db} = \pm 20n \log \omega, \quad \angle H(j\omega) = \pm n90^\circ$$


1st Order Magnitude Response:  $H_{db} = \pm 20 \log |1 + j\omega|$

Standard form (zero):  $c(1 + j\omega\tau)$   $c$  is gain

Standard form (pole):  $\frac{1}{1 + j\omega\tau}$  Corner freq:  $\omega = \frac{1}{\tau}$

Max error (3 dB) at corner freq


	zero	pole
$\omega\tau < 1$	0 dB	0 dB
$\omega\tau = 1$	0 dB	0 dB
$\omega\tau > 1$	$20 \log \omega\tau$	$-20 \log \omega\tau$

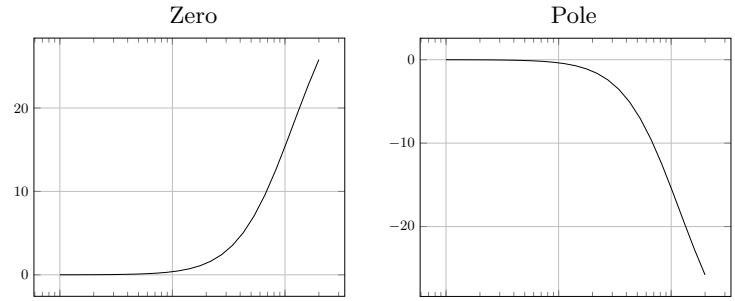

1st Order Phase Response:  $\angle H(j\omega) = \pm \angle(1 + j\omega\tau) = \arctan(\omega\tau)$

Connect  $\frac{1}{10\tau} < \omega < \frac{10}{\tau}$  w/ straight line.

	zero	pole
$\omega\tau \leq 0.1$	$0^\circ$	$0^\circ$
$\omega\tau = 1$	$+45^\circ$	$-45^\circ$
$\omega\tau > 10$	$+90^\circ$	$-90^\circ$
$0.1 < \omega\tau < 10$	$+45^\circ/\text{dec}$	$-45^\circ/\text{dec}$

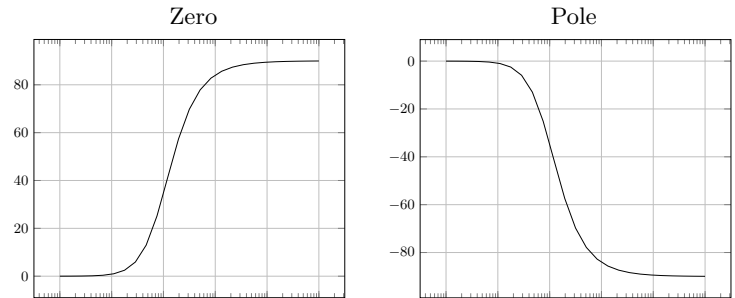

2nd Order Magnitude Response:  $H_{db} = \pm 20 \log |1 - (\omega\tau)^2 + j2\zeta(\omega\tau)|$

Standard form:  $H(j\omega) = 1 + 2\zeta(j\omega\tau) + (j\omega\tau)^2$

$$s^2 + 2\zeta\omega_0 s + \omega_0^2 = \left(\frac{s}{\omega_0}\right)^2 + 2\zeta\left(\frac{s}{\omega_0}\right) + 1 = 0, \quad s = j\omega$$

Corner freq:  $\omega_0 = 1/\tau \Rightarrow H_{db} = \pm 20 \log(2\zeta)$

	Complex conj zeros	Complex conj poles
$\omega\tau \ll 1$	0 dB	0 dB
$\omega\tau = 1$	$20 \log 2\zeta$	$-20 \log 2\zeta$
$\omega\tau \gg 1$	$+40 \text{ dB/dec}$	$-40 \text{ dB/dec}$
Btw regions	Depends on $\zeta$	Depends on $\zeta$

2nd Order Phase Response:  $\angle H(j\omega) = \arctan\left(\frac{2\zeta(\omega\tau)}{1 - (\omega\tau)^2}\right)$

	Complex conj zeros	Complex conj poles
$\omega\tau \ll 1$	$0^\circ$	$0^\circ$
$\omega\tau = 1$	$+90^\circ$	$-90^\circ$
$\omega\tau \gg 1$	$+180^\circ$	$-180^\circ$
Btw regions	Depends on $\zeta$	Depends on $\zeta$

## Laplace Transforms

$$\mathcal{L}[f(t)] = \int_{0^-}^{\infty} f(t)e^{-st} dt = F(s)$$

$$\mathcal{L}^{-1}[F(s)] = \frac{1}{2\pi j} \int_{\sigma_1 - j\infty}^{\sigma_1 + j\infty} F(s)e^{st} ds = f(t)$$

$$\mathcal{L}[f'] = sF(s) - f(0)$$

$$\mathcal{L}[f''] = s^2 F(s) - sf(0) - f'(0)$$

$$\mathcal{L}[u(t)] = \frac{1}{s}$$

$$\mathcal{L}[u(t - t_0)] = \frac{e^{-st_0}}{s}$$

$$\mathcal{L}[p(t)] = \frac{1 - e^{-st_0}}{s}$$

$$\mathcal{L}[\delta(t)] = 1$$

$$\mathcal{L}[\delta(t - t_0)] = e^{-st_0}$$

$$\text{IVT: } \lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} sF(s)$$

$$\text{FVT: } \lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$$

Poles of  $F(s)$  on LHS of  $s$ -plane (except poles at  $s = 0$ )

### Partial Fraction Expansion

$$\text{Real \& distinct roots: } \frac{P(s)}{Q(s)} = \frac{K_1}{s + p_1} + \cdots + \frac{K_j}{s + p_j} + \cdots + \frac{K_n}{s + p_n}$$

$$K_j = \frac{P(s)}{Q(s)}(s + p_j)|_{s = -p_j}$$

$$\mathcal{L}^{-1}\left[\frac{P(s)}{Q(s)}\right] = u(t) (K_1 e^{-p_1 t} + \cdots + K_j e^{-p_j t} + \cdots + K_n e^{-p_n t})$$

$$\text{Distinct complex roots: } \frac{P(s)}{Q(s)} = \frac{K}{s + (\alpha - j\beta)} + \frac{K^*}{s + (\alpha + j\beta)} + \cdots$$

$$K = \frac{P(s)}{Q(s)}(s + \alpha - j\beta)|_{s = -(\alpha - j\beta)} = |K| \angle \theta_K$$

$$\mathcal{L}^{-1}\left[\frac{P(s)}{Q(s)}\right] = u(t) [2|K|e^{-\alpha t} \cos(\beta t + \theta_K) + \cdots]$$



$$\text{Repeated real roots: } \frac{P(s)}{Q(s)} = \frac{K_1}{(s + p)^n} + \frac{K_2}{(s + p)^{n-1}} + \cdots + \frac{K_n}{s + p}$$

$$K_j = \frac{1}{(j-1)!} \left[ \frac{d^{(j-1)}}{ds^{(j-1)}} (s + p)^n F(s) \right]_{s = -p}$$
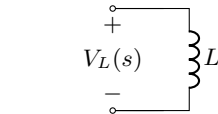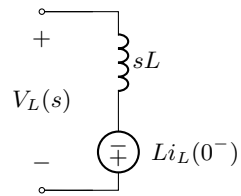
### Laplace Domain Model of Inductor

$$\mathcal{L}\{v_L(t)\} = V_L(s) = L[sI_L(s) - i_L(0^-)]$$



$$\mathcal{L}\{i_L(t)\} = I_L(s) = \frac{V_L(s)}{sL} + \frac{i_L(0^-)}{s}$$


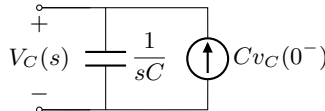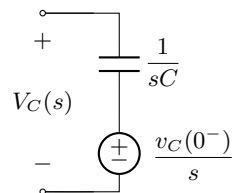
### Laplace Domain Model of Capacitor

$$\mathcal{L}\{i_C(t)\} = I_C(s) = C[sV_C(s) - v_C(0^-)]$$

$$\mathcal{L}\{v_C(t)\} = \frac{I_C(s)}{sC} + \frac{v_C(0^-)}{s}$$



## Impulse Response


$$Y(s) = H(s)X(s)$$

$$x(t) = \delta(t) \implies \mathcal{L}[\delta(t)] = 1 \implies y(t) = \mathcal{L}^{-1}[H(s)] = h(t)$$

$$\text{Given } h(t), y(t) = \mathcal{L}^{-1}[\mathcal{L}[h(t)]\mathcal{L}[x(t)]]$$


### Op-Amps

#### Assumptions

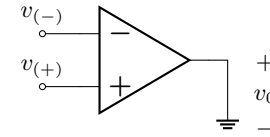

1.  $i_{(+)} = i_{(-)} = 0$
2.  $v_{(+)} - v_{(-)} = 0$
3. Gain  $A \approx \infty \implies v_{(+)} = v_{(-)}$
4.  $\beta \approx \infty \implies A = \text{const}$

### Inverting Amplifier

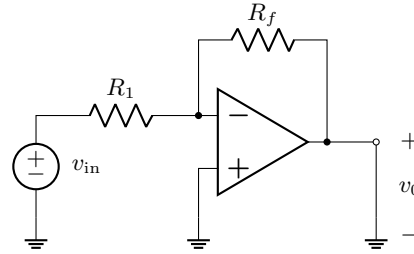


$$\frac{v_0}{v_{in}} = -\frac{R_f}{R_1} = A_f$$

$$v_0 = A_f v_{in}$$

$A_f$  called closed-loop (feedback) gain


### Non-Inverting Amplifier

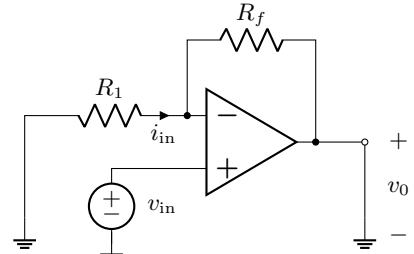

$$\frac{0 - v_{in}}{R_1} = \frac{v_{in} - v_0}{R_f}$$

$$\frac{v_0}{v_{in}} = 1 + \frac{R_f}{R_1} = A_f$$

### Voltage Follower (Unity Gain Buffer)

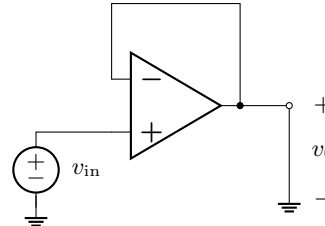


$$R_f = 0 \Omega, R_1 \rightarrow \infty$$

$$v_0 = v_{in}$$

$$A_f = 1$$


### Summing Amplifier

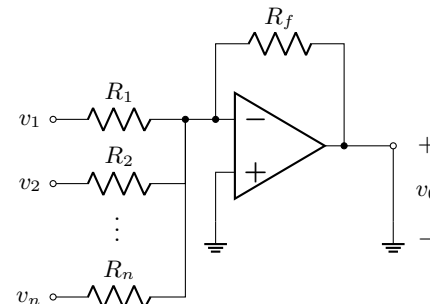

$$\frac{v_1 - 0}{R} + \frac{v_n - 0}{R} + \cdots + \frac{v_n - 0}{R} = \frac{0 - v_0}{R_f}$$

$$v_0 = -\frac{R_f}{R} (v_1 + v_2 + \cdots + v_n)$$

### Difference Amplifier

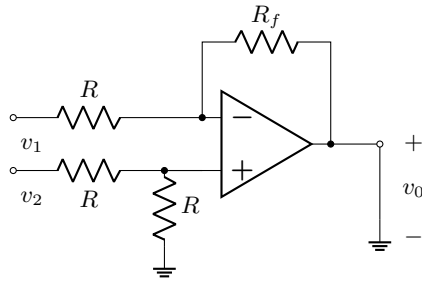


$$v_{(+)} = \frac{v_2}{2} = v_{(-)}$$

$$i_1 = \frac{v_1 - v_2/2}{R}$$

$$v_0 = \frac{v_2}{2} - i_1 R$$


$$v_0 = v_2 - v_1$$

### Differentiator

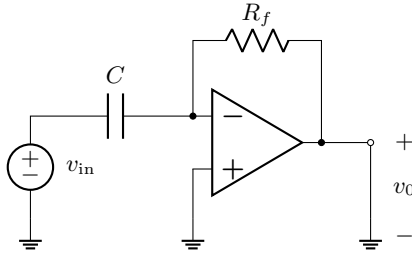

$$i_{in} = i_f = C \frac{dv_{in}}{dt} = \frac{0 - v_0}{R_f} \Rightarrow v_0 = -R_f C \frac{dv_{in}}{dt}$$

### Integrator

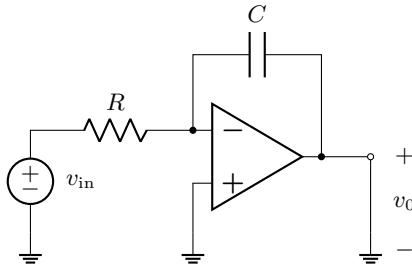


$$\frac{v_{in}}{R} = -C \frac{dv_0}{dt} \Rightarrow v_0 = -\frac{1}{RC} \int_0^t v_{in}(x) dx$$

### Non-Ideal Op-Amps

$$\frac{v_0}{v_s} = \frac{1}{1 + \frac{R_i}{R_0 + A R_i}} \quad A \rightarrow \infty \text{ for ideal case } (v_0/v_s = 1)$$

$$v_0 = A(v_{(+)} - v_{(-)}) = A\Delta v, \quad i_{in} = \Delta v/R_i$$

### Comparator

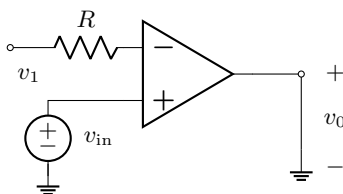

$$v_0 = A(v_{ref} - v_{in})$$


For  $E^+$  and  $E^-$  to op-amp,

$$v_{ref} > v_{in} \Rightarrow v_0 = E^+$$

$$v_{ref} < v_{in} \Rightarrow v_0 = E^-$$

Since  $A$  is large, any diff in  $v_{ref}$  and  $v_{in}$  will drive o/p to saturation.

### Diode

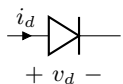


$$i_D = I_S (e^{qv_0(t)/(nkT)} - 1)$$

If  $v < 0$ , diode acts as open circuit ( $i = 0$ ); diode is reverse-biased.

If  $v > 0$ , diode acts as short circuit ( $v = 0$ ); diode is forward-biased.


### Half-Wave Voltage Rectifier

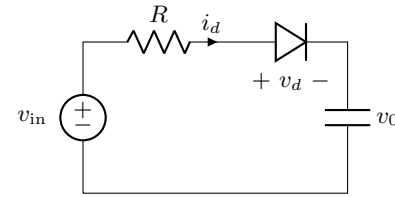

Diode conducts when  $v_d = v_{in} - v_0 > 0 \Rightarrow v_{in} > v_0$

$$i_{d, \max} = \frac{v_{in, \max} - v_0}{R}$$


### Full-Wave Voltage Rectifier

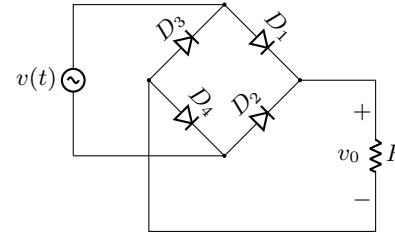


$$v(t) = V_m \sin \omega t$$

$$v_0 = \begin{cases} v_{in}, & v_{in} > 0 \\ -v_{in}, & v_{in} < 0 \end{cases}$$

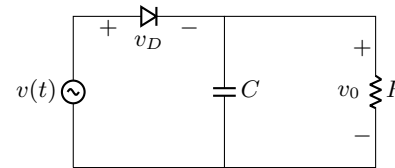
### Diode Rectification w/ Capacitive O/P Filter



### Diodes as Logic Circuits

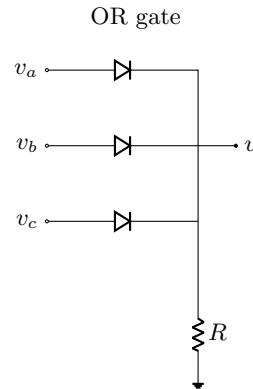


### AND gate

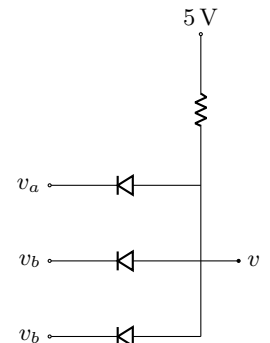

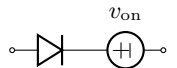
### Non-Ideal Diode Models

Const-voltage model:  $v_D = v_{on}$  in FB region




Src-resistor model:  $v_D = v_{on} + i_D R_D$  in FB region

$$P = i v_D + i^2 R_D$$

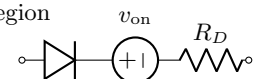

### Precision Half-Wave Rectifier

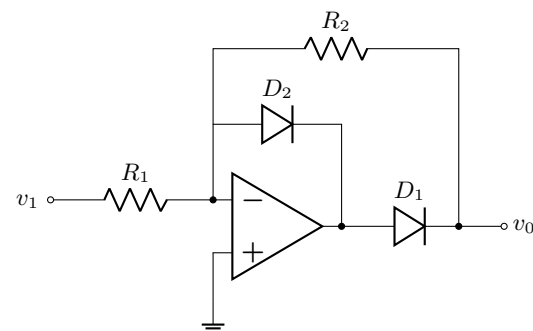


$v_1 > 0$ :  $D_1$  RB and  $D_2$  FB  $\Rightarrow v_0 = 0$  ( $i$  to  $v_0$  ground)

$v_1 < 0$ :  $D_1$  FB and  $D_2$  RB  $\Rightarrow v_0 = -\frac{R_2}{R_1}v_1$  ( $i$  to  $v_1$  ground)

.....


*LPF*

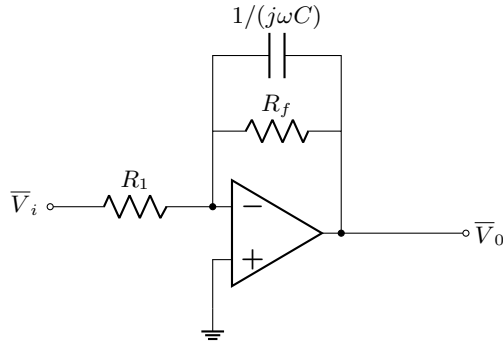

$$\frac{\bar{V}_0}{\bar{V}_i} = -\frac{R_f}{R_1} \left( \frac{1}{1 + j\omega R_f C} \right)$$

.....

## Two Port Networks

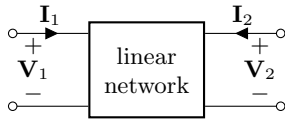

.....

### Admittance Parameters

$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{y}_{11} & \mathbf{y}_{12} \\ \mathbf{y}_{21} & \mathbf{y}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} \quad \mathbf{y}_{11} = \left. \frac{\mathbf{I}_1}{\mathbf{V}_1} \right|_{\mathbf{V}_2=0} \quad \mathbf{y}_{12} = \left. \frac{\mathbf{I}_1}{\mathbf{V}_2} \right|_{\mathbf{V}_1=0}$$

$$\mathbf{y}_{21} = \left. \frac{\mathbf{I}_2}{\mathbf{V}_1} \right|_{\mathbf{V}_2=0} \quad \mathbf{y}_{22} = \left. \frac{\mathbf{I}_2}{\mathbf{V}_2} \right|_{\mathbf{V}_1=0}$$

All units in [S]

$$\mathbf{I}_1 = \mathbf{y}_{11}\mathbf{V}_1 + \mathbf{y}_{12}\mathbf{V}_2$$

$$\mathbf{I}_2 = \mathbf{y}_{21}\mathbf{V}_1 + \mathbf{y}_{22}\mathbf{V}_2$$

Can also compute by finding currents using nodal analysis.

$\mathbf{y}_{11}$ : short circuit i/p admittance

$\mathbf{y}_{22}$ : short circuit o/p admittance

$\mathbf{y}_{12}$ ,  $\mathbf{y}_{21}$ : short circuit transfer admittance

.....

### Impedance Parameters

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} \quad \mathbf{z}_{11} = \left. \frac{\mathbf{V}_1}{\mathbf{I}_1} \right|_{\mathbf{I}_2=0} \quad \mathbf{z}_{12} = \left. \frac{\mathbf{V}_1}{\mathbf{I}_2} \right|_{\mathbf{I}_1=0}$$

$$\mathbf{z}_{21} = \left. \frac{\mathbf{V}_2}{\mathbf{I}_1} \right|_{\mathbf{I}_2=0} \quad \mathbf{z}_{22} = \left. \frac{\mathbf{V}_2}{\mathbf{I}_2} \right|_{\mathbf{I}_1=0}$$

All units in [ $\Omega$ ]

$$\mathbf{V}_1 = \mathbf{z}_{11}\mathbf{I}_1 + \mathbf{z}_{12}\mathbf{I}_2$$

$$\mathbf{V}_2 = \mathbf{z}_{21}\mathbf{I}_1 + \mathbf{z}_{22}\mathbf{I}_2$$

$\mathbf{z}_{11}$ : short circuit i/p impedance

$\mathbf{z}_{22}$ : short circuit o/p impedance

$\mathbf{z}_{12}$ ,  $\mathbf{z}_{21}$ : short circuit transfer impedance

## Hybrid Parameters

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{h}_{11} & \mathbf{h}_{12} \\ \mathbf{h}_{21} & \mathbf{h}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{V}_2 \end{bmatrix} \quad \mathbf{h}_{11} = \left. \frac{\mathbf{V}_1}{\mathbf{I}_1} \right|_{\mathbf{V}_2=0} \quad \mathbf{h}_{12} = \left. \frac{\mathbf{V}_1}{\mathbf{V}_2} \right|_{\mathbf{I}_1=0}$$

$$\mathbf{h}_{21} = \left. \frac{\mathbf{I}_2}{\mathbf{I}_1} \right|_{\mathbf{V}_2=0} \quad \mathbf{h}_{22} = \left. \frac{\mathbf{I}_2}{\mathbf{V}_2} \right|_{\mathbf{I}_1=0}$$

$$\mathbf{V}_1 = \mathbf{h}_{11}\mathbf{I}_1 + \mathbf{h}_{12}\mathbf{V}_2$$

$$\mathbf{I}_2 = \mathbf{h}_{21}\mathbf{I}_1 + \mathbf{h}_{22}\mathbf{V}_2$$

$\mathbf{h}_{11}$ : short circuit input impedance [ $\Omega$ ]

$\mathbf{h}_{22}$ : open circuit input admittance [S]

$\mathbf{h}_{12}$ : open circuit input reverse  $V$  gain [pu]

$\mathbf{h}_{21}$ : short circuit forward  $I$  gain [pu]

.....

## Transmission (ABCD) Parameters

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = \begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix} \begin{bmatrix} \mathbf{V}_2 \\ -\mathbf{I}_2 \end{bmatrix} \quad \mathbf{A} = \left. \frac{\mathbf{V}_1}{\mathbf{V}_2} \right|_{\mathbf{I}_2=0} \quad \mathbf{B} = -\left. \frac{\mathbf{V}_1}{\mathbf{I}_2} \right|_{\mathbf{V}_2=0}$$

$$\mathbf{C} = \left. \frac{\mathbf{I}_1}{\mathbf{V}_2} \right|_{\mathbf{I}_2=0} \quad \mathbf{D} = \left. \frac{\mathbf{I}_1}{\mathbf{I}_2} \right|_{\mathbf{V}_2=0}$$

$$\mathbf{V}_1 = \mathbf{A}\mathbf{V}_2 - \mathbf{B}\mathbf{I}_2$$

$$\mathbf{I}_1 = \mathbf{C}\mathbf{V}_2 - \mathbf{D}\mathbf{I}_2$$

$\mathbf{A}$ : open circuit  $V$  ratio [pu]

$\mathbf{B}$ : -ve short circuit transfer impedance [ $\Omega$ ]

$\mathbf{C}$ : open circuit transfer admittance [S]


$\mathbf{D}$ : -ve short circuit  $I$  ratio [pu]

.....
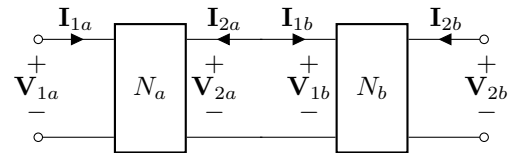
## Cascading Two Port Networks


Most conveniently modelled using ABCD parameters.

$$\begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix} = \begin{bmatrix} \mathbf{A}_a & \mathbf{B}_a \\ \mathbf{C}_a & \mathbf{D}_a \end{bmatrix} \begin{bmatrix} \mathbf{A}_b & \mathbf{B}_b \\ \mathbf{C}_b & \mathbf{D}_b \end{bmatrix}$$



.....

## Thevenin Equivalent System

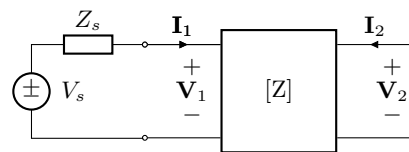

$$\begin{cases} \mathbf{V}_1 = \mathbf{I}_1\mathbf{z}_{11} + \mathbf{I}_2\mathbf{z}_{12} \\ \mathbf{V}_2 = \mathbf{I}_1\mathbf{z}_{21} + \mathbf{I}_2\mathbf{z}_{22} \\ \mathbf{V}_s = \mathbf{V}_1 + \mathbf{I}_1\mathbf{z}_s \end{cases} \Rightarrow \mathbf{I}_1 = \frac{\mathbf{V}_s - \mathbf{I}_2\mathbf{z}_{12}}{\mathbf{z}_s + \mathbf{z}_{11}}$$

$$\mathbf{V}_2 = \underbrace{\frac{\mathbf{z}_{21}}{\mathbf{z}_{11} + \mathbf{z}_s}}_{\mathbf{V}_{th}} \mathbf{V}_s + \underbrace{\left( \mathbf{z}_{22} - \frac{\mathbf{z}_{12}\mathbf{z}_{21}}{\mathbf{z}_{11} + \mathbf{z}_s} \right)}_{\mathbf{z}_{th}} \mathbf{I}_2$$

Operation	Time domain	Laplace domain
Scaling	$f(at), \quad a \geq 0$	$\frac{1}{a}F\left(\frac{s}{a}\right)$
Time convolution	$f_1(t) * f_2(t)$	$F_1(s)F_2(s)$
Time differentiation	$\frac{df}{dt}$	$sF(s) - f(0^-)$
	$\frac{d^2f}{dt^2}$	$s^2F(s) - sf(0^-) - f'(0^-)$
	$\frac{d^3f}{dt^3}$	$s^3F(s) - s^2f(0^-) - sf'(0^-) - f''(0^-)$
Time integration	$\int_{0^-}^t f(x) \, dx$	$\frac{1}{s}F(s)$
	$\int_{-\infty}^t f(x) \, dx$	$\frac{1}{s}F(s) + \frac{1}{s} \int_{-\infty}^{0^-} f(t) \, dt$
Time shift	$f(t - t_0)u(t - t_0)$	$F(s)e^{-st_0}, \quad t_0 \geq 0$
Frequency shift	$f(t)e^{s_0t}$	$F(s - s_0)$
Frequency differentiation	$-tf(t)$	$\frac{dF(s)}{ds}$
Initial value thm	$f(0^+)$	$\lim_{s \rightarrow \infty} sF(s)$
Final value thm	$\lim_{t \rightarrow \infty} f(t)$	$\lim_{s \rightarrow 0} sF(s)$
		(poles of $sF(s)$ in LHP)

*Unilateral LT of Important Functions*

	$f(t)$	$F(s)$		$f(t)$	$F(s)$
1	$\delta(t)$	1	7	$t^n e^{\lambda t} u(t)$	$\frac{n!}{(s - \lambda)^{n+1}}$
2	$u(t)$	$\frac{1}{s}$	8	$\cos(bt)u(t)$	$\frac{s}{s^2 + b^2}$
3	$tu(t)$	$\frac{1}{s^2}$	9	$\sin(bt)u(t)$	$\frac{b}{s^2 + b^2}$
4	$t^n u(t)$	$\frac{n!}{s^{n+1}}$	10	$e^{-at} \cos(bt)u(t)$	$\frac{s + a}{(s + a)^2 + b^2}$
5	$e^{\lambda t} u(t)$	$\frac{1}{s - \lambda}$	11	$e^{-at} \sin(bt)u(t)$	$\frac{b}{(s + a)^2 + b^2}$
6	$te^{\lambda t} u(t)$	$\frac{1}{(s - \lambda)^2}$			

$\Delta \equiv$  determinant

$\begin{bmatrix} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{bmatrix}$	$\frac{1}{\Delta Y} \begin{bmatrix} \mathbf{y}_{11} & -\mathbf{y}_{12} \\ -\mathbf{y}_{21} & \mathbf{y}_{11} \end{bmatrix}$	$\frac{1}{\mathbf{C}} \begin{bmatrix} \mathbf{A} & \Delta T \\ \mathbf{1} & \mathbf{D} \end{bmatrix}$	$\frac{1}{\mathbf{h}_{22}} \begin{bmatrix} \Delta H & \mathbf{h}_{12} \\ -\mathbf{h}_{21} & 1 \end{bmatrix}$
<hr/>			
$\frac{1}{\Delta Z} \begin{bmatrix} \mathbf{z}_{22} & -\mathbf{z}_{12} \\ -\mathbf{z}_{21} & \mathbf{z}_{11} \end{bmatrix}$	$\begin{bmatrix} \mathbf{y}_{11} & \mathbf{y}_{12} \\ \mathbf{y}_{21} & \mathbf{y}_{22} \end{bmatrix}$	$\frac{1}{\mathbf{B}} \begin{bmatrix} \mathbf{D} & -\Delta T \\ -1 & \mathbf{A} \end{bmatrix}$	$\frac{1}{\mathbf{h}_{11}} \begin{bmatrix} 1 & -\mathbf{h}_{12} \\ \mathbf{h}_{21} & \Delta H \end{bmatrix}$
<hr/>			
$\frac{1}{\mathbf{z}_{21}} \begin{bmatrix} \mathbf{z}_{11} & \Delta Z \\ 1 & \mathbf{z}_{22} \end{bmatrix}$	$-\frac{1}{\mathbf{y}_{21}} \begin{bmatrix} \mathbf{y}_{22} & 1 \\ \Delta Y & \mathbf{y}_{11} \end{bmatrix}$	$\begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix}$	$-\frac{1}{\mathbf{h}_{21}} \begin{bmatrix} \Delta H & \mathbf{h}_{11} \\ \mathbf{h}_{22} & 1 \end{bmatrix}$
<hr/>			
$\frac{1}{\mathbf{z}_{22}} \begin{bmatrix} \Delta Z & \mathbf{z}_{12} \\ -\mathbf{z}_{21} & 1 \end{bmatrix}$	$\frac{1}{\mathbf{y}_{11}} \begin{bmatrix} 1 & -\mathbf{y}_{12} \\ \mathbf{y}_{21} & \Delta Y \end{bmatrix}$	$\frac{1}{\mathbf{D}} \begin{bmatrix} \mathbf{B} & \Delta T \\ -1 & \mathbf{C} \end{bmatrix}$	$\begin{bmatrix} \mathbf{h}_{11} & \mathbf{h}_{12} \\ \mathbf{h}_{21} & \mathbf{h}_{22} \end{bmatrix}$